

Introduction to Electrical Engg.
EE 103
Assignment – 4

Q1. Consider the circuit shown in Figure 1. Perform nodal analysis and hence determine V_A , V_B , V_C . Also determine the power delivered by the current source.

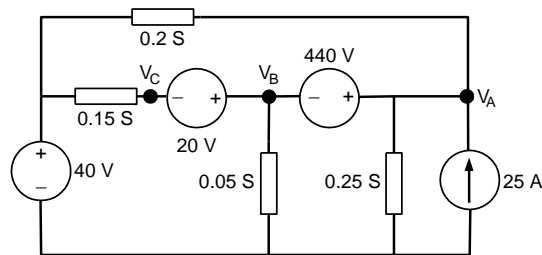


Figure 1

Q2. In the circuit shown in Figure 2, $V_{s1} = -10$ V, $I_{s2} = 1$ A, and all resistors are $10\ \Omega$. Apply nodal analysis to determine V_A , V_B , V_C .

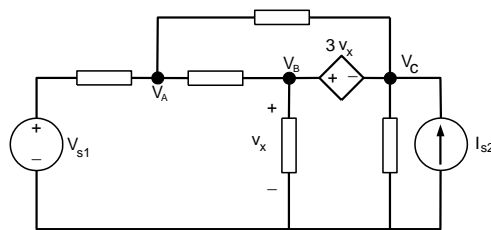


Figure 2

Q3. Consider the circuit shown in Figure 3 along with the defined loops 1, 2 and 3. Determine I_1 , I_2 , I_3 and hence determine, v .

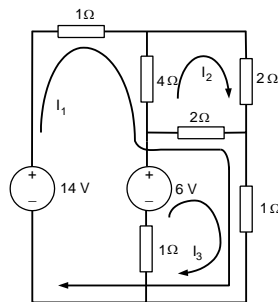


Figure 3

Q4. Consider the circuit shown in Figure 4, wherein $V_{s1} = 250 \text{ V}$ and $I_{s2} = 0.75 \text{ A}$. Write two mesh equations and hence determine V_B .

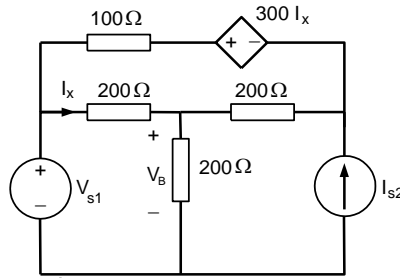


Figure 4

Q5. Consider the linear network of Figure 5. Two separate dc measurements are taken. In the first experiment it is found that when $V_a = 7 \text{ V}$ and $I_b = 3 \text{ A}$, the load current is $I_{\text{load}} = 3 \text{ A}$. In the second experiment it found that when $V_a = 7 \text{ V}$ and $I_b = 1 \text{ A}$, then $I_{\text{load}} = 3 \text{ A}$. Compute I_{load} when $V_a = 15 \text{ V}$ and $I_b = 9 \text{ A}$.

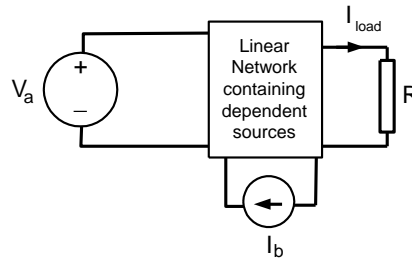


Figure 5

Q6. Find the Thevenin equivalent circuit of the network shown in Figure 6 as viewed from A - B

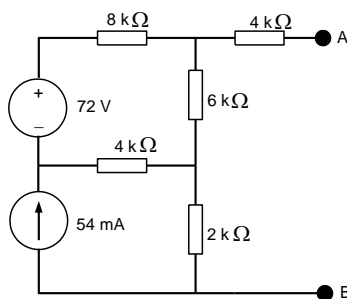


Figure 6

Q7. Find Thevenin equivalent of the circuit shown in Figure 7 as viewed from A – B. What is the Norton's equivalent?

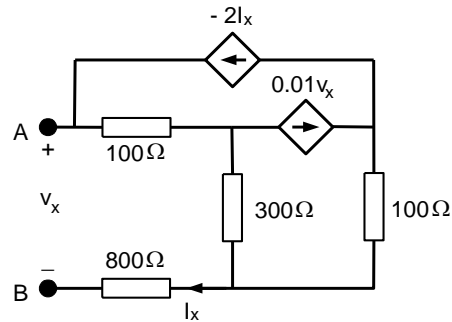


Figure 7

Q8. Find the Norton and Thevenin equivalent of the circuit shown in Figure 8.

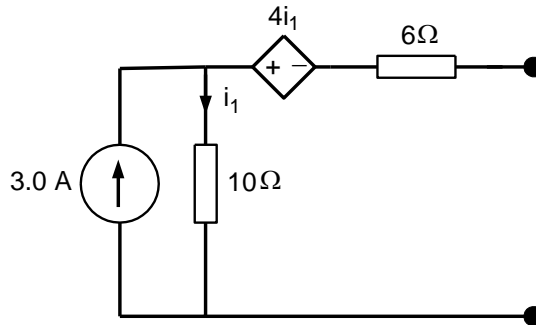


Figure 8

Q9. For the circuit shown in Figure 9, find the load resistance, R_L needed for maximum power transfer. Also determine the maximum power delivered to the load resistor, R_L .


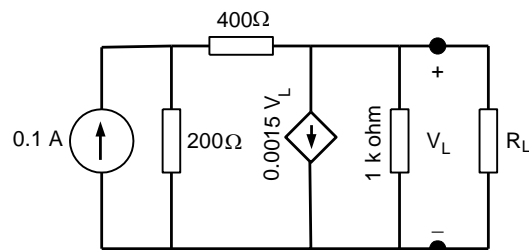



Figure 9

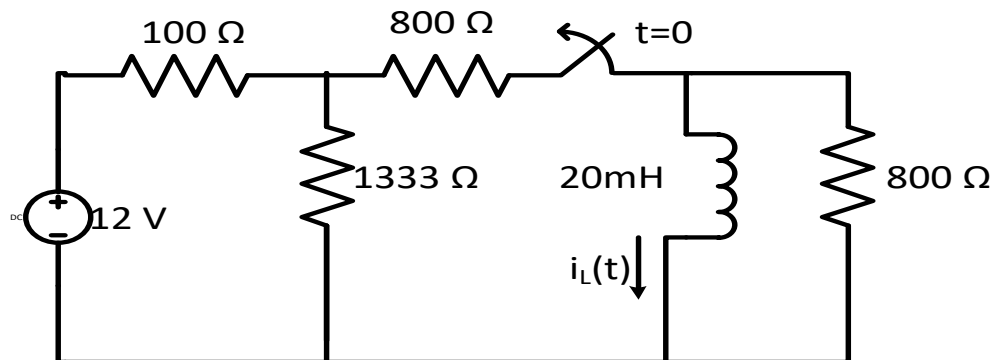10) In the Figure the 12 V source has been applied for a long time before the switch opens at $t = 0$. Find $i_L(0^+)$ and $i_L(t)$ for $t > 0$. Sketch $i_L(t)$ for $0 \leq t \leq 5\tau$, where τ is the circuit time constant for $t > 0$.



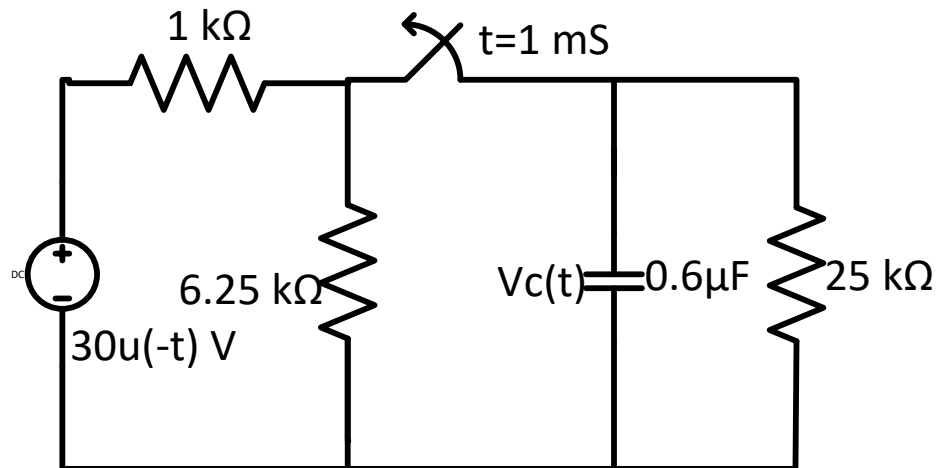11) In the figure the 30 V source has been applied for a long time, and the switch is opened at $t=1$ ms.

- Find $v_c(0^+)$ and $v_c(t)$ for $0 < t < 1$ ms.
- Find $v_c(1^+ \text{ ms})$ and $v_c(t)$ for $t \leq 1$ ms.
- Find $v_c(t)$ for $0 \leq t \leq 25$ ms.



- For the circuit of Figure A find $v_c(t)$ for $t > 0$, assuming that the 80 V source has been applied for a very long time. Plot the response $v_c(t)$ for $0 \leq t \leq 0.25$ s.
- Consider now the circuit of Figure B. Find $v_c(t)$ for $t > 0$. Plot the response $v_c(t)$ for $0 \leq t \leq 0.25$ s.
- Compare the time constants of the circuit of part (a) and (b) for the intervals $0 \leq t \leq 60$ ms and $60 \text{ ms} \leq t$.

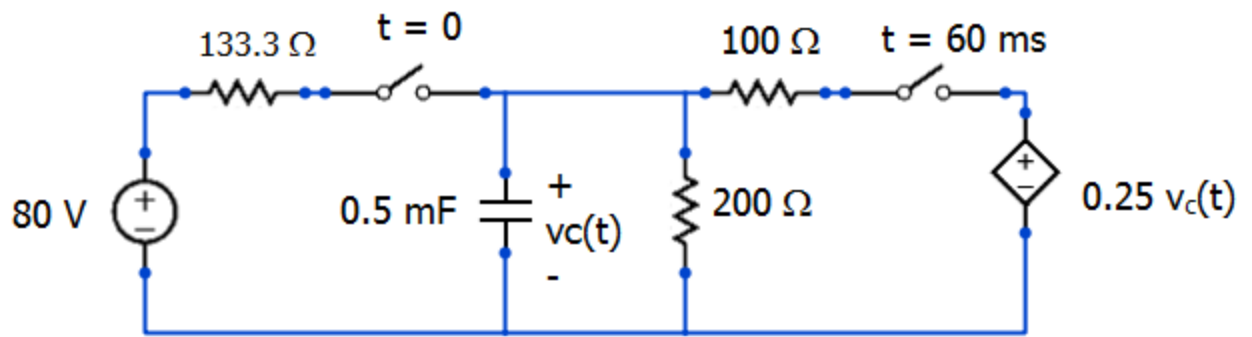


Figure **A**

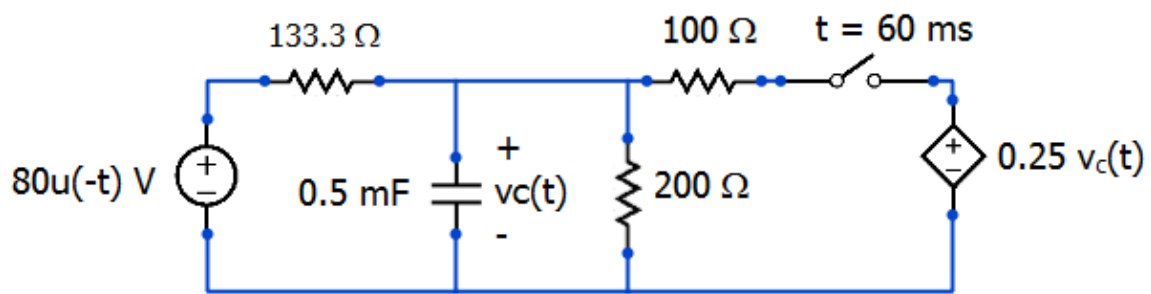


Figure **B**